

Міністерство освіти і науки України
Національний університет «Львівська політехніка»



Звіт

про виконання лабораторної роботи №2

з дисципліни: «Моделювання комп'ютерних систем»

На тему: «Структурний опис цифрового автомата. Перевірка роботи автомата за допомогою стенда Elbert V2 – Spartan 3A FPGA.»

Варіант - 4

Виконала:

ст.гр. КІ-202

Максимчук К.С.

Прийняв:

Козак Н.Б.

Львів 2023

Мета роботи: на базі стенда Elbert V2 – Spartan 3A FPGA реалізувати цифровий автомат світлових ефектів згідно вимог.

Завдання згідно з варіантом:

Варіант – 4:

- Пристрій повинен реалізувати 8 комбінацій вихідних сигналів згідно таблиці:

Стан#	LED_0	LED_1	LED_2	LED_3	LED_4	LED_5	LED_6	LED_7
0	1	0	0	0	0	0	0	1
1	0	1	0	0	0	0	1	0
2	0	0	1	0	0	1	0	0
3	0	0	0	1	1	0	0	0
4	0	0	1	1	1	1	0	0
5	0	1	1	1	1	1	1	0
6	1	1	1	1	1	1	1	1
7	0	0	0	0	0	0	0	0

- Пристрій повинен використовувати 12MHz тактовий сигнал від мікроконтролера IC1 і знижувати частоту за допомогою внутрішнього подільника. Мікроконтролер IC1 є частиною стенда Elbert V2 – Spartan 3A FPGA. Тактовий сигнал заведено на вхід LOC = P129 FPGA (див. Додаток – 1).
- Інтерфейс пристрою повинен мати вхід синхронного скидання (RESET).
- Інтерфейс пристрою повинен мати вхід керування режимом роботи (MODE):
 - Якщо MODE=0 то стан пристрою інкрементується по зростаючому фронту тактового сигналу пам'яті станів (0->1->2->3->4->5->6->7->0...).
 - Якщо MODE=1 то стан пристрою декрементується по зростаючому фронту тактового сигналу пам'яті станів (0->7->6->5->4->3->2->1->0...).
- Інтерфейс пристрою повинен мати однорозрядний вхід керування швидкістю роботи (SPEED):
 - Якщо SPEED=0 то автомат працює зі швидкістю, визначеною за замовчуванням.
 - Якщо SPEED=1 то автомат працює зі швидкістю, В 4 РАЗИ НИЖЧОЮ ніж в режимі (SPEED= 0).
- Для керування сигналом MODE використати будь який з 8 DIP перемикачів (див. Додаток – 1).
- Для керування сигналами RESET/SPEED використати будь які з PUSH BUTTON кнопок (див. Додаток – 1).

Виконання роботи:

1. Створив проект.
2. Додав VHDL Module для імплементації логіки формування вихідних сигналів.

Код OutputLogic:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity out_logic_intf is2
    Port ( IN_BUS : in  std_logic_vector(2 downto 0);
          OUT_BUS : out std_logic_vector(7 downto 0)
          );
end out_logic_intf;

architecture out_logic_arch of out_logic_intf is

begin

    OUT_BUS(0) <= ((not(IN_BUS(2)) and not(IN_BUS(1)) and not(IN_BUS(0))) or (IN_BUS(2) and
IN_BUS(1) and not(IN_BUS(0))));

    OUT_BUS(1) <= ((not(IN_BUS(2)) and not(IN_BUS(1)) and IN_BUS(0)) or (IN_BUS(2) and not
(IN_BUS(1)) and IN_BUS(0)) or (IN_BUS(2) and IN_BUS(1) and not(IN_BUS(0))));

    OUT_BUS(2) <= ((not(IN_BUS(2)) and IN_BUS(1) and not(IN_BUS(0))) or (IN_BUS(2) and
not(IN_BUS(1)) and not(IN_BUS(0))) or (IN_BUS(2) and not (IN_BUS(1)) and IN_BUS(0)) or (IN_BUS(2) and
IN_BUS(1) and not(IN_BUS(0))));

    OUT_BUS(3) <= ((not(IN_BUS(2)) and IN_BUS(1) and IN_BUS(0)) or (IN_BUS(2) and not(IN_BUS(1))
and not(IN_BUS(0))) or (IN_BUS(2) and not (IN_BUS(1)) and IN_BUS(0)) or (IN_BUS(2) and IN_BUS(1) and
not(IN_BUS(0))));

    OUT_BUS(4) <= ((not(IN_BUS(2)) and IN_BUS(1) and IN_BUS(0)) or (IN_BUS(2) and not(IN_BUS(1))
and not(IN_BUS(0))) or (IN_BUS(2) and not (IN_BUS(1)) and IN_BUS(0)) or (IN_BUS(2) and IN_BUS(1) and
not(IN_BUS(0))));

    OUT_BUS(5) <= ((not(IN_BUS(2)) and IN_BUS(1) and not(IN_BUS(0))) or (IN_BUS(2) and
not(IN_BUS(1)) and not(IN_BUS(0))) or (IN_BUS(2) and not (IN_BUS(1)) and IN_BUS(0)) or (IN_BUS(2) and
IN_BUS(1) and not(IN_BUS(0))));
```

```
OUT_BUS(6) <= ((not(IN_BUS(2)) and not(IN_BUS(1)) and IN_BUS(0)) or (IN_BUS(2) and not
(IN_BUS(1)) and IN_BUS(0)) or (IN_BUS(2) and IN_BUS(1) and not(IN_BUS(0))));
```

```
OUT_BUS(7) <= ((not(IN_BUS(2)) and not(IN_BUS(1)) and not(IN_BUS(0))) or (IN_BUS(2) and
IN_BUS(1) and not(IN_BUS(0))));
```

```
end out_logic_arch;
```

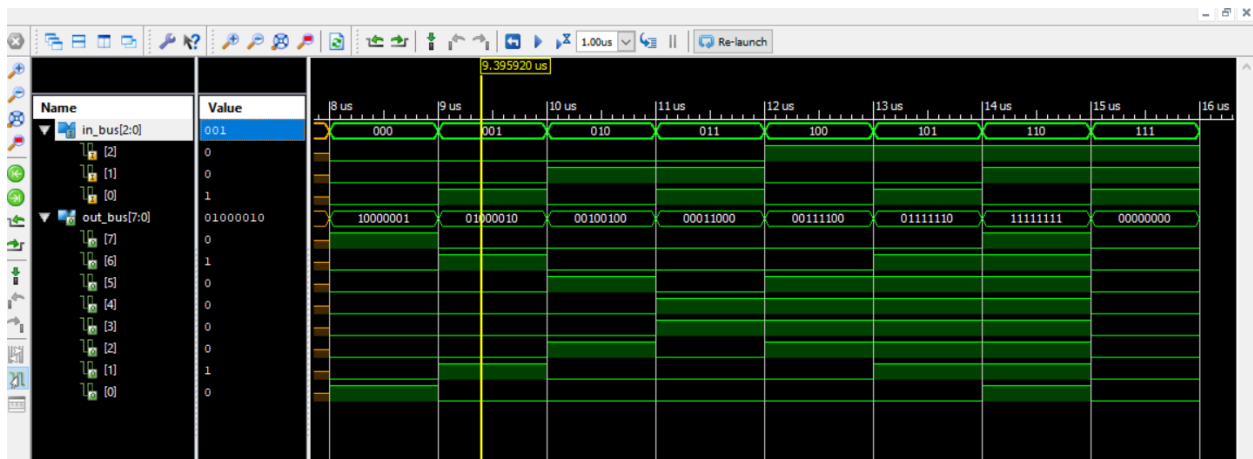


Рис. 1 Діаграма проведеної симуляції для OutputLogic

3. Додав VHDL Module для імплементації логіки формування переходів. ***Kod TransitionLogic:***

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity transition_logic_intf is
```

```
Port ( CUR_STATE : in std_logic_vector(2 downto 0);
```

```
MODE : in std_logic;
```

```
RES : in std_logic;
```

```
NEXT_STATE : out std_logic_vector(2 downto 0)
```

```
);
```

```
end transition_logic_intf;
```

```
architecture transition_logic_arch of transition_logic_intf is
```

begin

NEXT_STATE(0) <= (not(RES) and not(MODE) and not(CUR_STATE(2)) and not(CUR_STATE(1)) and not(CUR_STATE(0))) or -- 000 -> 001

(not(RES) and not(MODE) and not(CUR_STATE(2)) and CUR_STATE(1) and not(CUR_STATE(0))) or -- 010 -> 011

(not(RES) and not(MODE) and CUR_STATE(2) and not(CUR_STATE(1)) and not(CUR_STATE(0))) or -- 100 -> 101

(not(RES) and not(MODE) and CUR_STATE(2) and CUR_STATE(1) and not(CUR_STATE(0))) or -- 110 -> 111

(not(RES) and MODE and not(CUR_STATE(2)) and (CUR_STATE(1)) and not(CUR_STATE(0))) or -- 001 <- 010

(not(RES) and MODE and (CUR_STATE(2)) and not(CUR_STATE(1)) and not(CUR_STATE(0))) or -- 011 <- 100

(not(RES) and MODE and CUR_STATE(2) and (CUR_STATE(1)) and not(CUR_STATE(0))) or -- 101 <- 110

(not(RES) and MODE and not(CUR_STATE(2)) and not(CUR_STATE(1)) and not(CUR_STATE(0))); -- 111 <- 000

NEXT_STATE(1) <= (not(RES) and not(MODE) and not(CUR_STATE(2)) and not(CUR_STATE(1)) and CUR_STATE(0)) or -- 001 -> 010

(not(RES) and not(MODE) and not(CUR_STATE(2)) and CUR_STATE(1) and not(CUR_STATE(0))) or -- 010 -> 011

(not(RES) and not(MODE) and CUR_STATE(2) and not(CUR_STATE(1)) and CUR_STATE(0)) or -- 101 -> 110

(not(RES) and not(MODE) and CUR_STATE(2) and CUR_STATE(1) and not(CUR_STATE(0))) or -- 110 -> 111

(not(RES) and MODE and not(CUR_STATE(2)) and (CUR_STATE(1)) and (CUR_STATE(0))) or -- 010 <- 011

(not(RES) and MODE and CUR_STATE(2) and not(CUR_STATE(1)) and not(CUR_STATE(0))) or -- 011 <- 100

(not(RES) and MODE and CUR_STATE(2) and CUR_STATE(1) and CUR_STATE(0)) or -- 110 <- 111

(not(RES) and MODE and not(CUR_STATE(2)) and not(CUR_STATE(1)) and not(CUR_STATE(0))); -- 111 <- 000

NEXT_STATE(2) <= (not(RES) and not(MODE) and not(CUR_STATE(2)) and CUR_STATE(1) and CUR_STATE(0)) or -- 011 -> 100

(not(RES) and not(MODE) and CUR_STATE(2) and not(CUR_STATE(1)) and not(CUR_STATE(0))) or -- 100 -> 101

(not(RES) and not(MODE) and CUR_STATE(2) and not(CUR_STATE(1)) and CUR_STATE(0)) or -- 101 -> 110

(not(RES) and not(MODE) and CUR_STATE(2) and CUR_STATE(1) and not(CUR_STATE(0))) or -- 110 -> 111

(not(RES) and MODE and CUR_STATE(2) and not(CUR_STATE(1)) and CUR_STATE(0)) or -- 100 <- 101

```

(not(RES) and MODE and CUR_STATE(2) and CUR_STATE(1) and not(CUR_STATE(0))) or -- 101 <- 110
(not(RES) and MODE and CUR_STATE(2) and CUR_STATE(1) and CUR_STATE(0)) or -- 110 <- 111
(not(RES) and MODE and not(CUR_STATE(2)) and not(CUR_STATE(1)) and
not(CUR_STATE(0))); -- 111 <- 000

```

end transition_logic_arch;

 


Рис. 2 Діаграма проведеної симуляції для TransitionLogic

4. Згенерував Schematic файли для OutputLogic та TransitionLogic.
5. Створив Schematic файл LightController, реалізував в ньому пам'ять стану автомата та зв'язав між собою всі його частини.

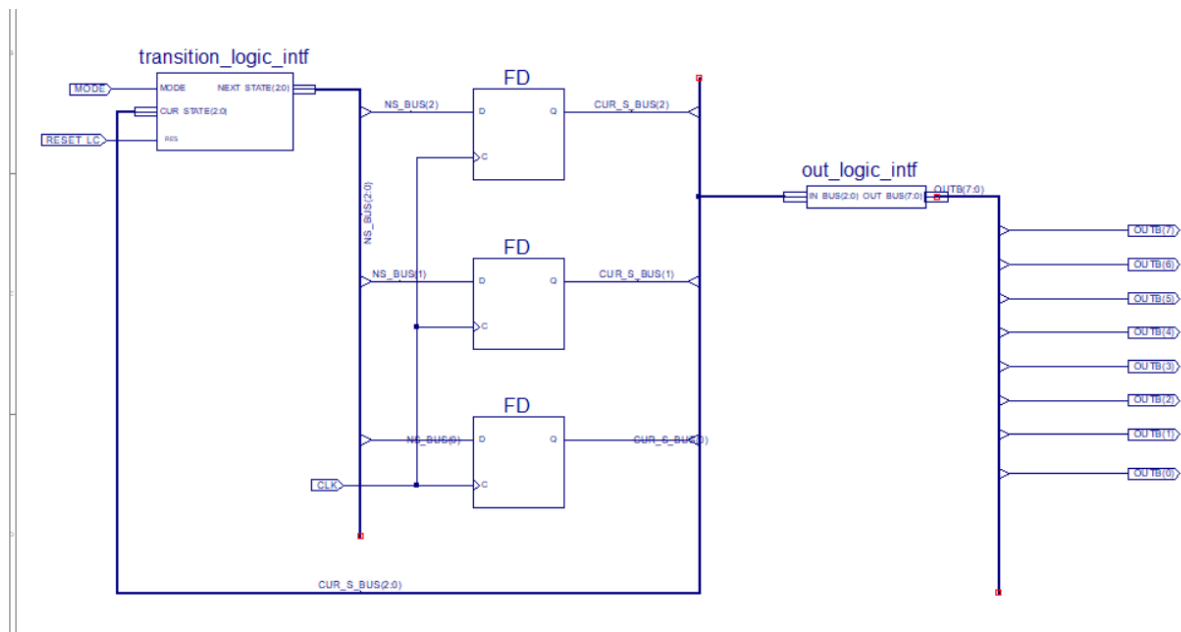


Рис. 3 Схема LightController

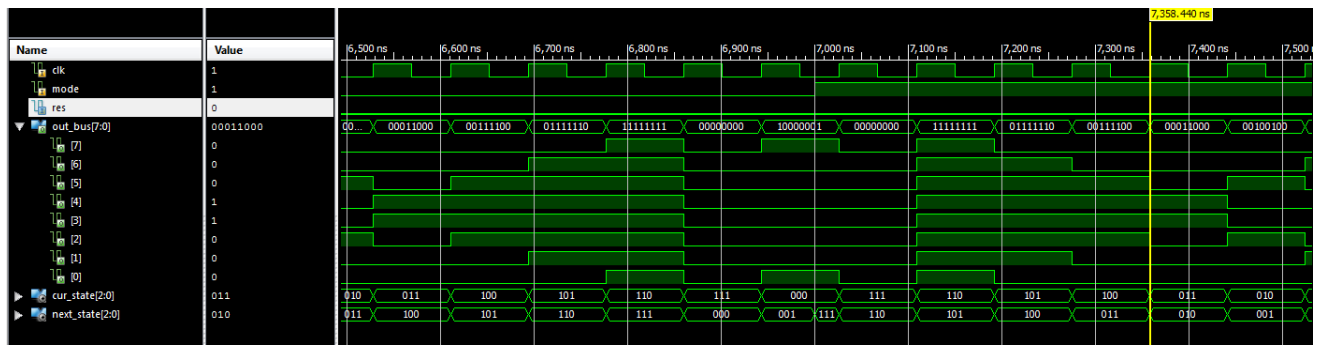


Рис. 4 Діаграма проведеної симуляції для LightController

6. Створив Schematic файл TopLevel, в якому реалізував подільник вхідної частоти та інтегрував його зі створеним автоматом, попередньо згенерувавши для нього Schematic файл.

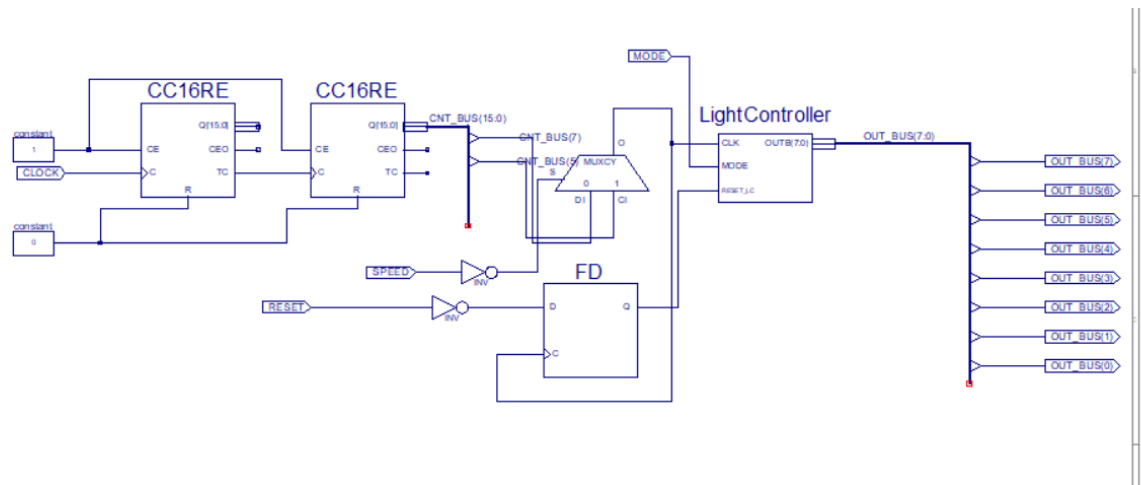


Рис. 5 Схема TopLevel

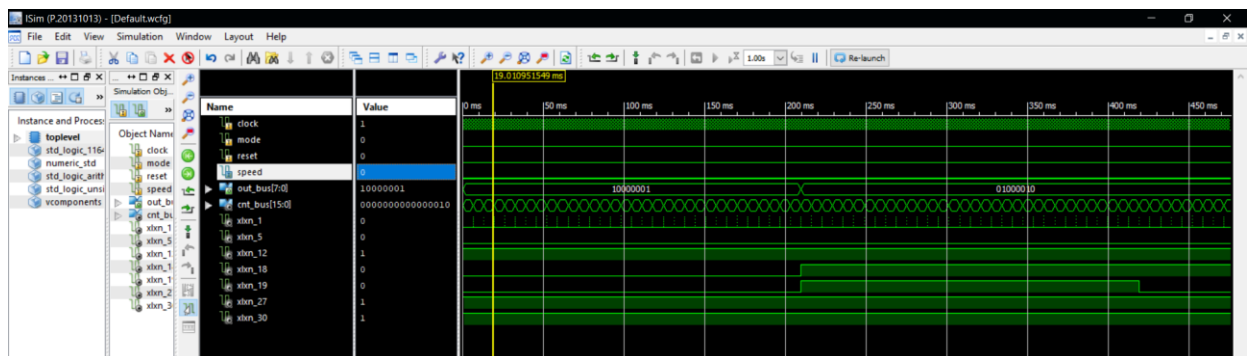


Рис. 6 Діаграма проведеної симуляції для TopLevel

7. Додав файл Constraints.ucf та призначив виводам схеми фізичної виводи FPGA.

```
#+++++
++++#
# This file is a .ucf for ElbertV2 Development Board
# To use it in your project :
# * Remove or comment the lines corresponding to unused pins in the project
# * Rename the used signals according to the your project
#+++++
++++#

#####
#####
# UCF for ElbertV2 Development Board
#####
#####
CONFIG VCCAUX = "3.3" ;

# Clock 12 MHz
NET "CLOCK" LOC = P129 | IOSTANDARD = LVCMOS33 | PERIOD = 12MHz;

#####
#####
# LED
#####
#####

NET "OUT_BUS(0)" LOC = P46 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
NET "OUT_BUS(1)" LOC = P47 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
NET "OUT_BUS(2)" LOC = P48 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
NET "OUT_BUS(3)" LOC = P49 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
NET "OUT_BUS(4)" LOC = P50 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE =
12;
NET "OUT_BUS(5)" LOC = P51 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
NET "OUT_BUS(6)" LOC = P54 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
NET "OUT_BUS(7)" LOC = P55 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;

#####
#####
# DP Switches
#####
#####

NET "MODE" LOC = P70 | PULLUP | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;

#####
#####
# Switches
#####
#####

NET "RESET" LOC = P80 | PULLUP | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE
= 12;
```



```
NET "SPEED"      LOC = P79  | PULLUP  | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE
= 12;
```

TestBench:

```
-- Vhdl test bench created from schematic C:\rubbish\MKS\2\Telegram Desktop\Lab_2\Lab_2\TopLevel.sch - Fri Apr
28 09:57:47 2023
```

```
--
```

```
-- Notes:
```

```
-- 1) This testbench template has been automatically generated using types
-- std_logic and std_logic_vector for the ports of the unit under test.
-- Xilinx recommends that these types always be used for the top-level
-- I/O of a design in order to guarantee that the testbench will bind
-- correctly to the timing (post-route) simulation model.
-- 2) To use this template as your testbench, change the filename to any
-- name of your choice with the extension .vhd, and use the "Source->Add"
-- menu in Project Navigator to import the testbench. Then
-- edit the user defined section below, adding code to generate the
-- stimulus for your design.
```

```
--
```

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
LIBRARY UNISIM;
USE UNISIM.Vcomponents.ALL;
ENTITY TopLevel_TopLevel_sch_tb IS
END TopLevel_TopLevel_sch_tb;
ARCHITECTURE behavioral OF TopLevel_TopLevel_sch_tb IS
```

```
    COMPONENT TopLevel
    PORT( CLOCK : IN STD_LOGIC;
          OUT_BUS : OUT STD_LOGIC_VECTOR (7 DOWNT0 0);
          MODE : IN STD_LOGIC;
          RESET : IN STD_LOGIC;
          SPEED : IN STD_LOGIC);
    END COMPONENT;
```

```
    SIGNAL CLOCK : STD_LOGIC := '0';
    SIGNAL OUT_BUS : STD_LOGIC_VECTOR (7 DOWNT0 0);
    SIGNAL MODE : STD_LOGIC;
    SIGNAL RESET : STD_LOGIC;
    SIGNAL SPEED : STD_LOGIC;
```

```
BEGIN
```

```
    UUT: TopLevel PORT MAP(
        CLOCK => CLOCK,
        OUT_BUS => OUT_BUS,
        MODE => MODE,
        RESET => RESET,
        SPEED => SPEED
    );
```

```
-- *** Test Bench - User Defined Section ***
```

```

tb : PROCESS
BEGIN
  -- Apply input stimuli to the design
  MODE <= '0';
  RESET <= '0';
  SPEED <= '0';
  wait for 1000 ms;

  MODE <= '1';
  RESET <= '1';
  SPEED <= '1';

  wait for 1000 ms;

  MODE <= '1';
  SPEED <= '0';

  wait for 1000 ms;

  MODE <= '1';
  SPEED <= '1';

  wait for 1000 ms;

  MODE <= '0';
  SPEED <= '1';

  wait for 1000 ms;

  MODE <= '0';
  SPEED <= '0';

  wait for 1000 ms;

  -- Add output check statements to verify the expected output
  --assert OUT_BUS = "00000000" report "Test failed: Output does not match expected value" severity error;


  WAIT; -- will wait forever
END PROCESS;
-- *** End Test Bench - User Defined Section ***

tb_clk : PROCESS
BEGIN

  CLOCK <= not CLOCK;
  wait for 83 ns;

END PROCESS;

END;
```

 

8. Згенерував бінарний файл для цифрового автомата світлових ефектів.

Висновок: виконавши лабораторну роботу, здобуто навички реалізації цифрових автоматів світлових ефектів.